

Microprocessors, Lecture 5

Memory Interfacing




Hamid Fadishei

Assistant Professor, University of Bojnord

Spring 2015


Types of Memory

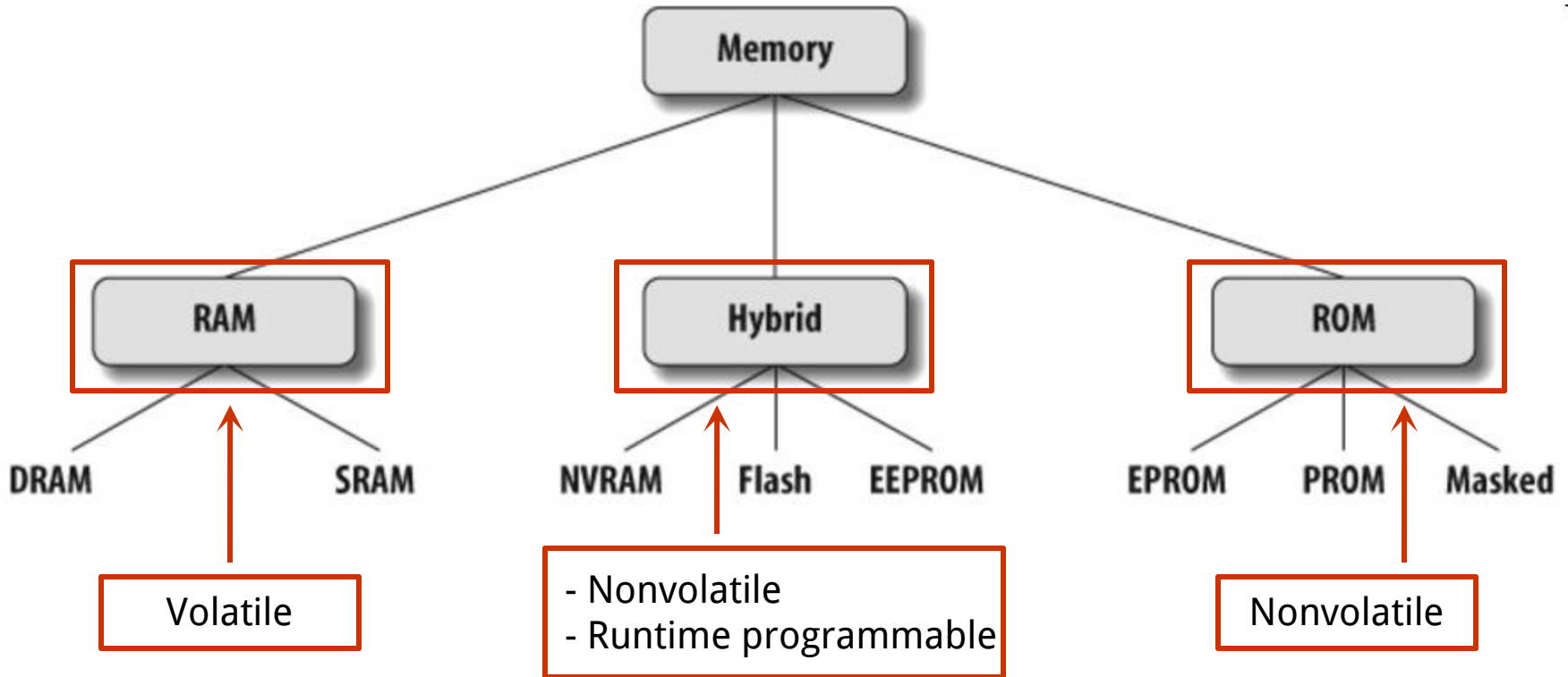


Volatile: loss of power => loss of data



Types of Memory

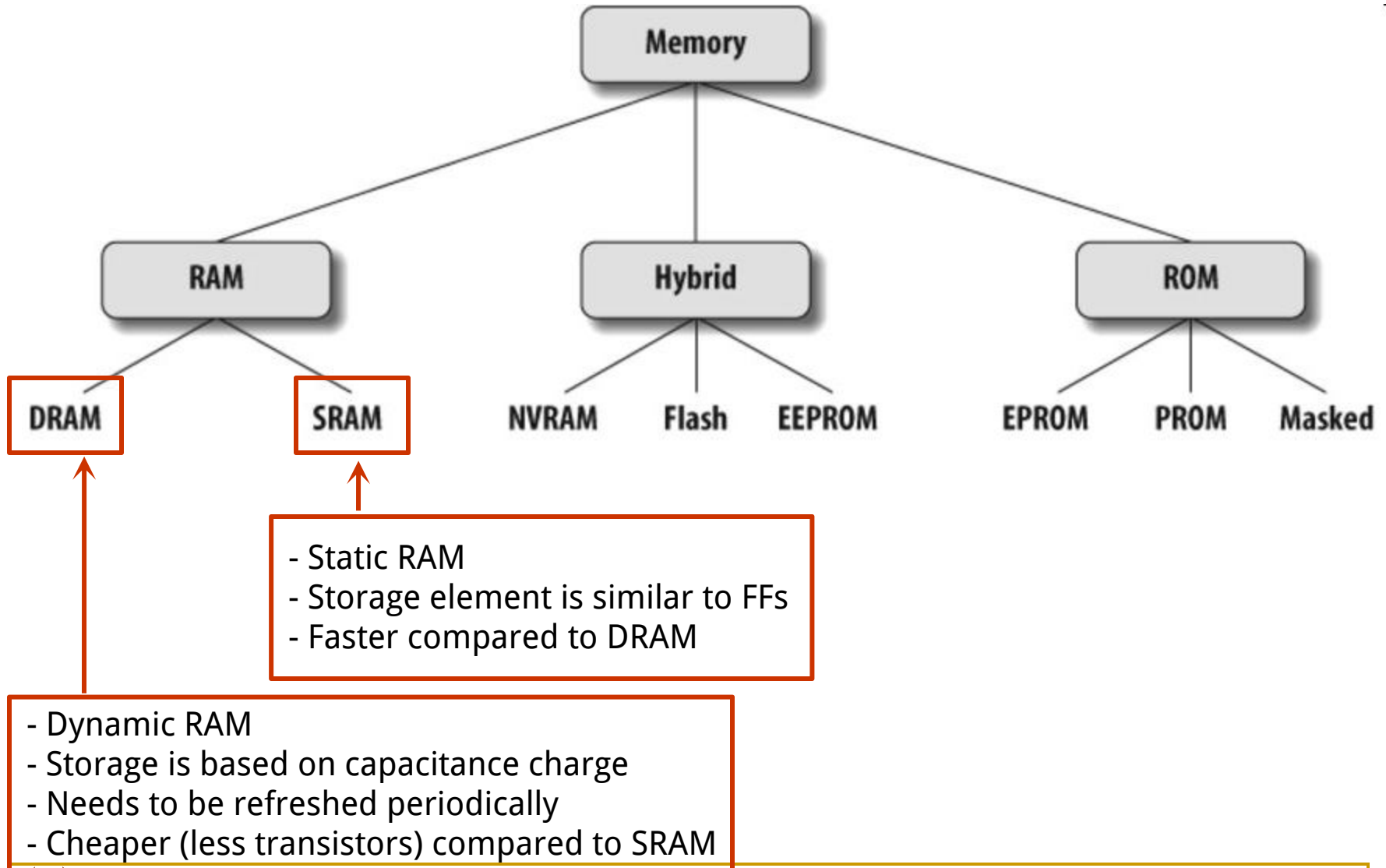


Types of Memory

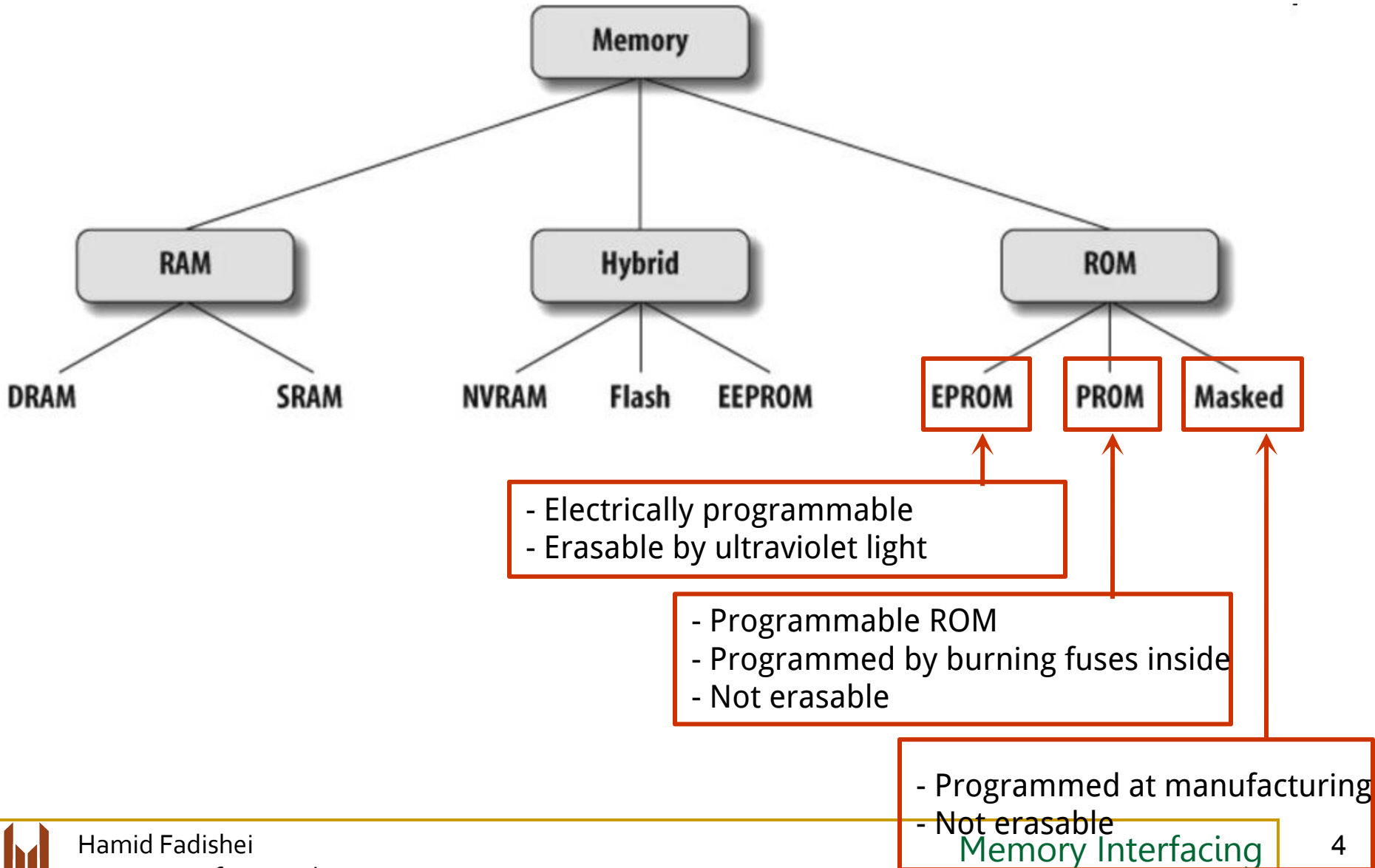

EPROM

Almost obsolete today!

 


EPROM

UV Eraser





www.old-computers.com

EPROM Programmer

 

Types of Memory

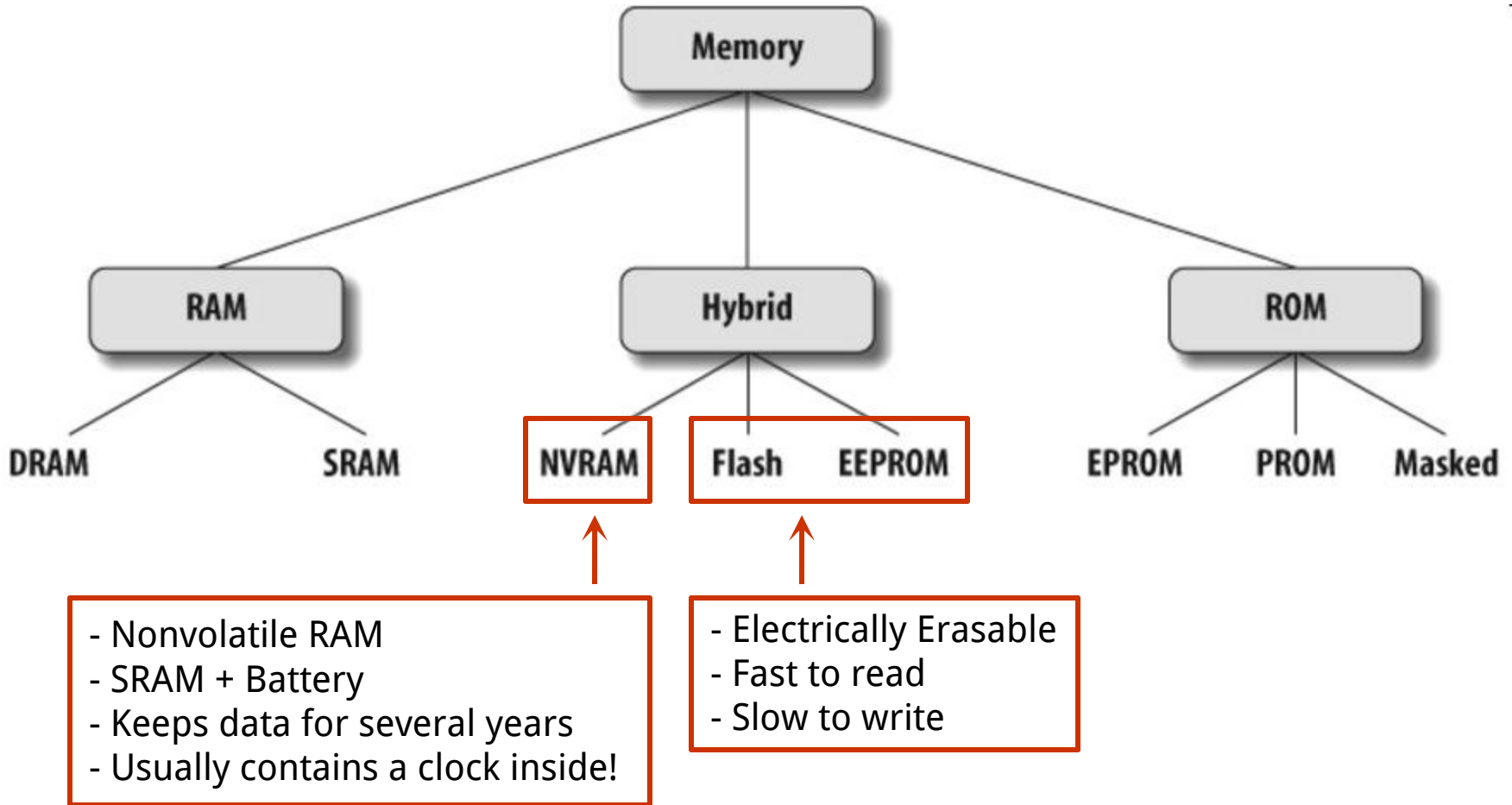


 

NVRAM



Flash

 

EEPROM



Serial EEPROM



Universal Programmer



Memory interfacing


- Question: How to interface a (Z80) microprocessor to a memory chip?
 - We should first answer these two questions:
 - How does Z80 works with memory?
 - How does the memory chip expect to be worked with?
- The requirements that should match
 - Timing
 - Electrical characteristics
 - Data format



- How does Z80 work with memory?
 - Z80 memory operations
 - Read
 - Places a 16 bit address on its address bar
 - Asserts MREQ to indicate address bus holds a valid address
 - Asserts RD to indicate that it wants to read
 - Write
 - Places a 16 bit address on its address bar
 - Asserts MREQ and places data on its data bus
 - Asserts WR signal


Z80 Side

- Z80 memory read timing

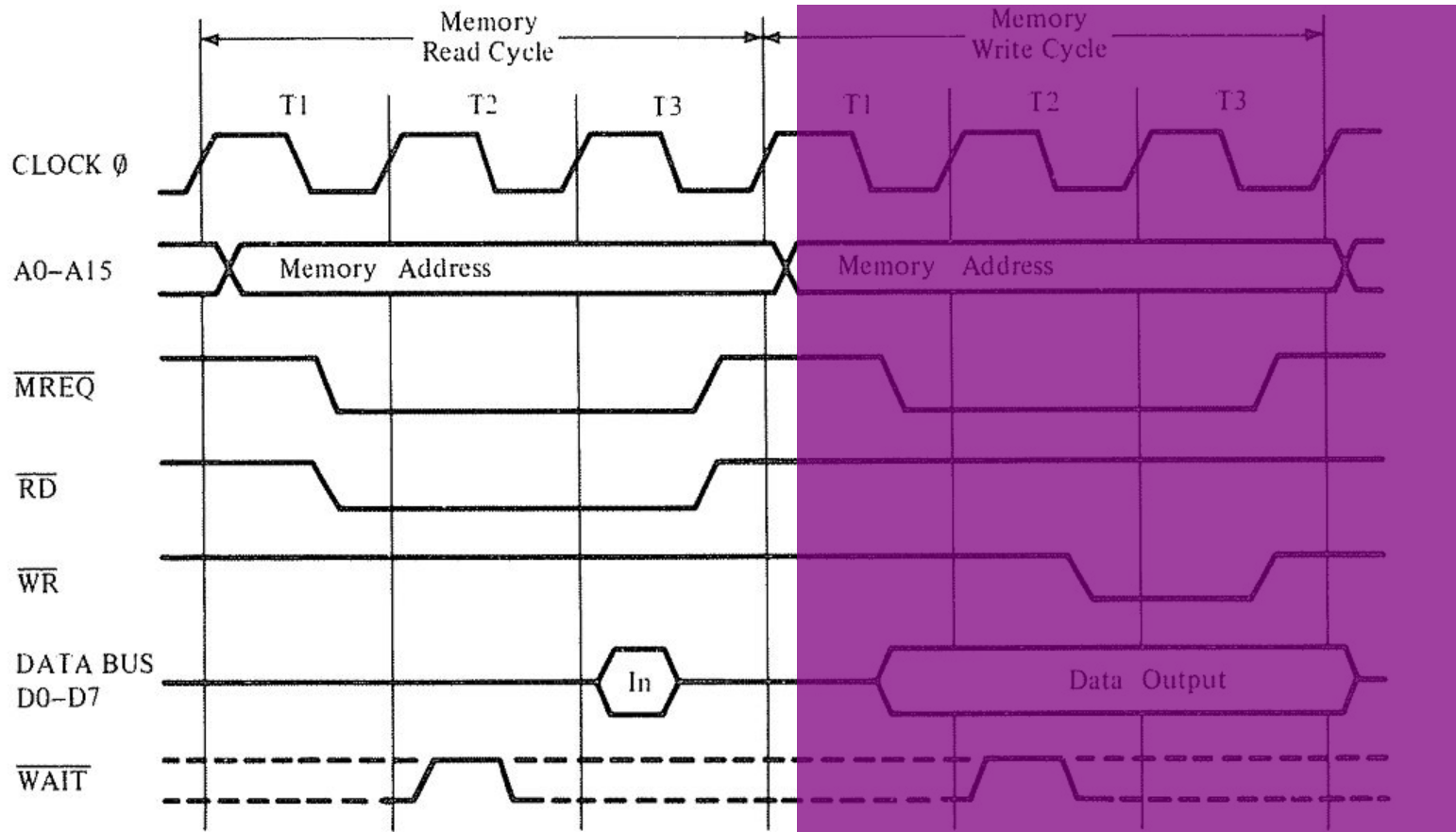


Z80 Side

- Z80 memory write timing

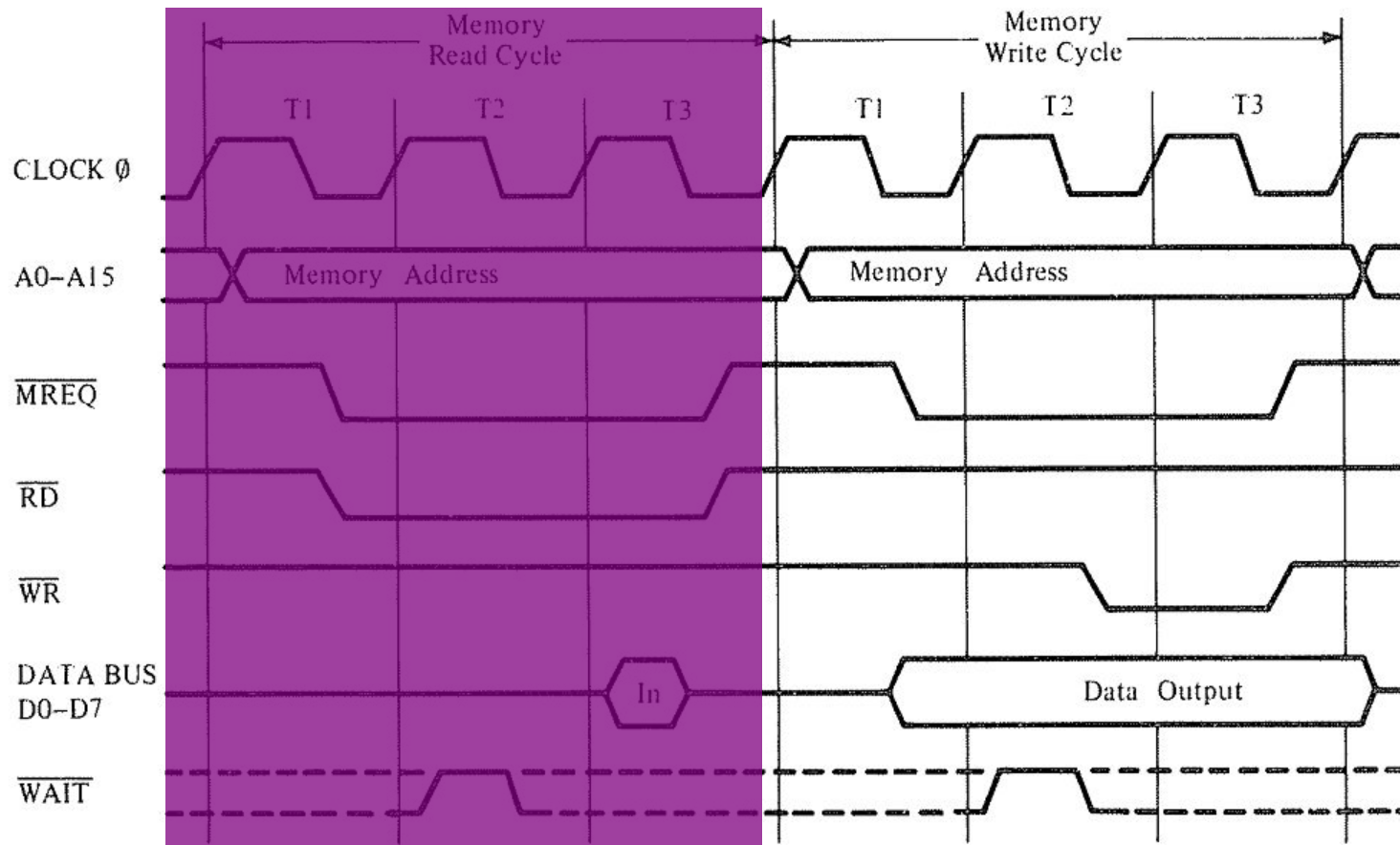


Memory side

 - Typical memory unit
 - Address pins
 - Data pins
 - Control pins
 - Chip select
 - Output enable
 - Write




Memory Side

- Memory read timing

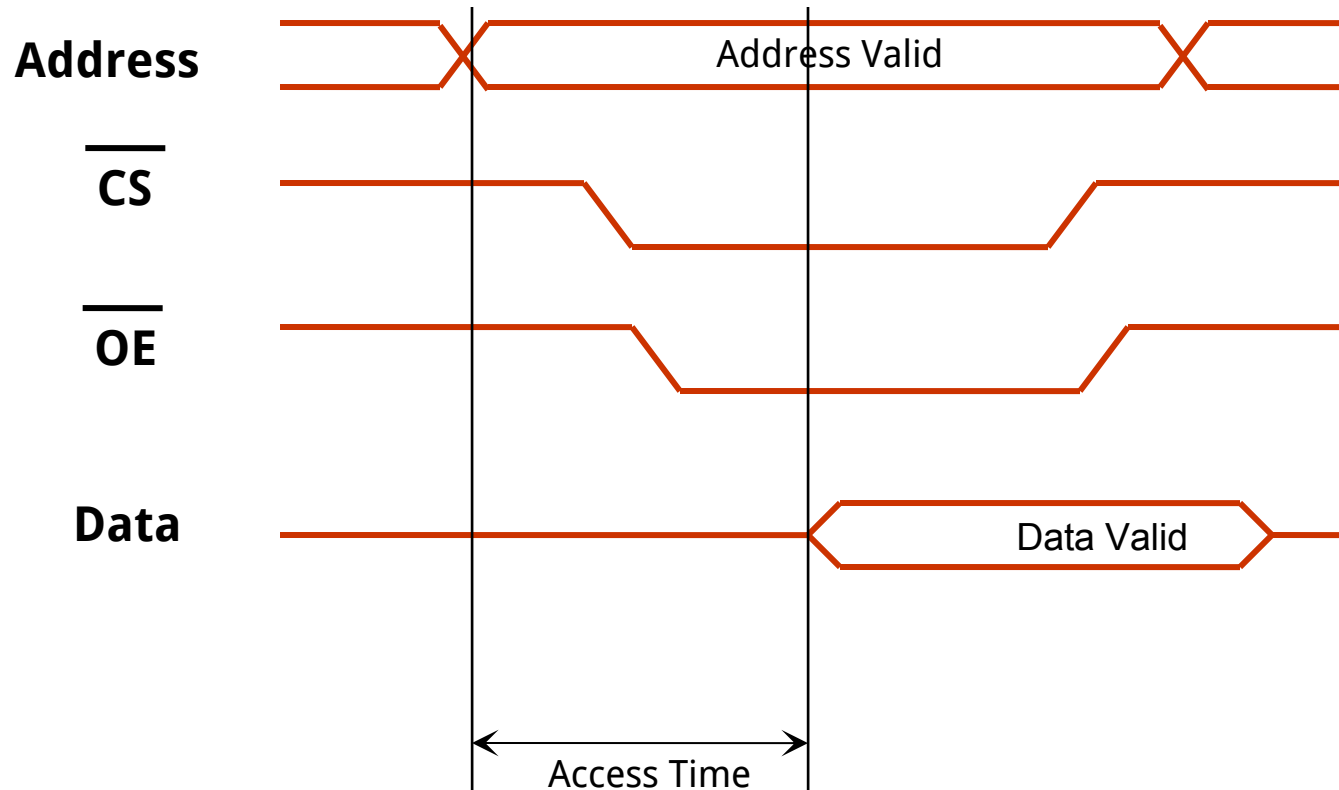


Memory Side

- Memory write timing

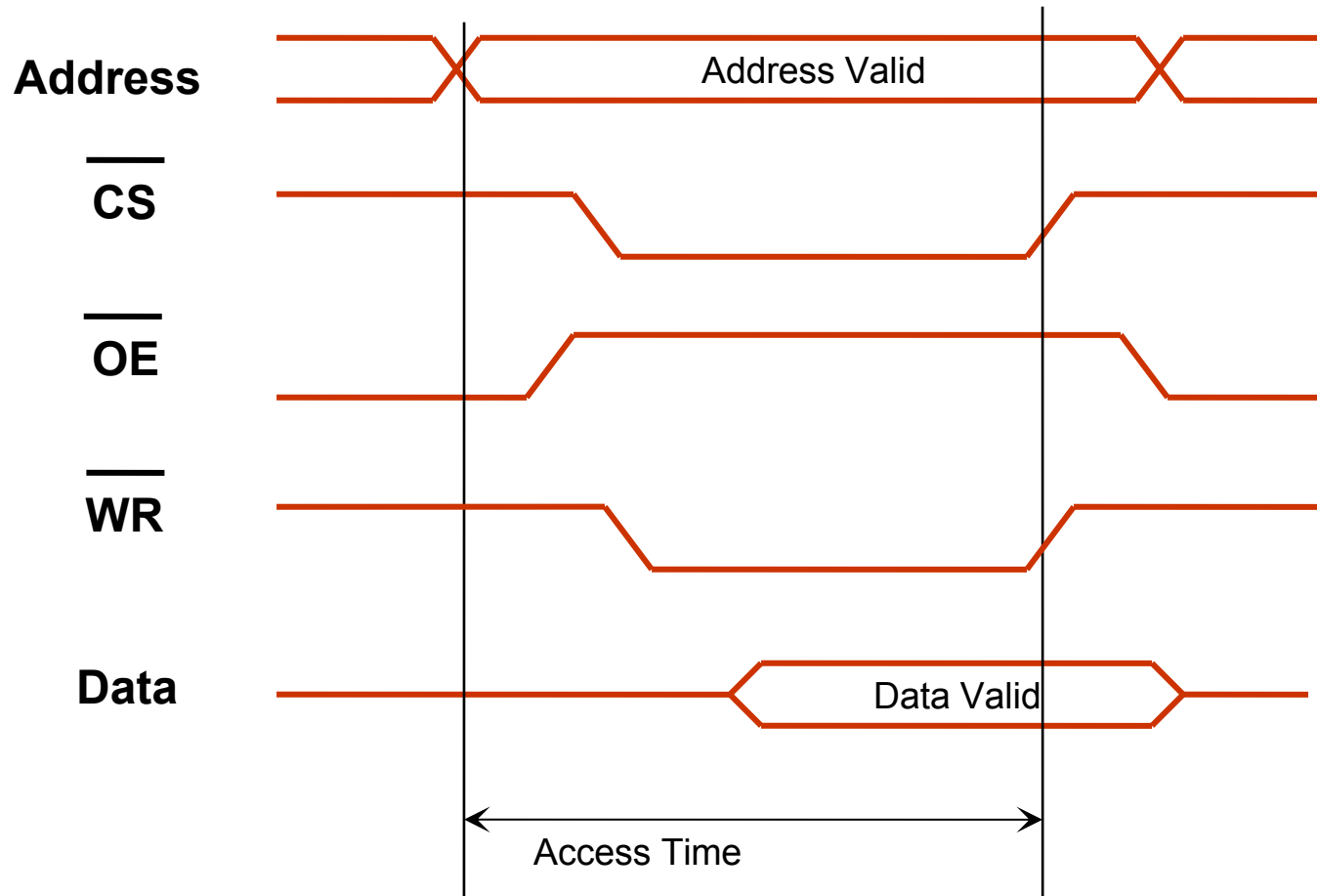


Z80 – Memory interconnection

- Interfacing memory to Z80

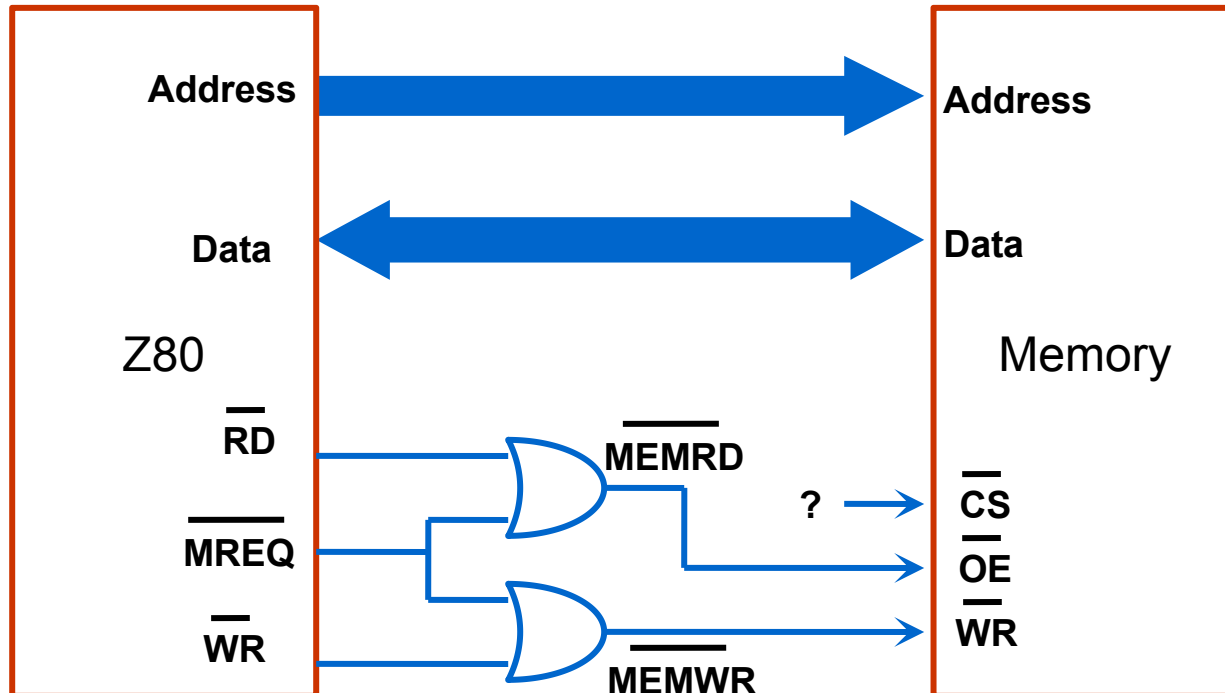


Memory Mapping

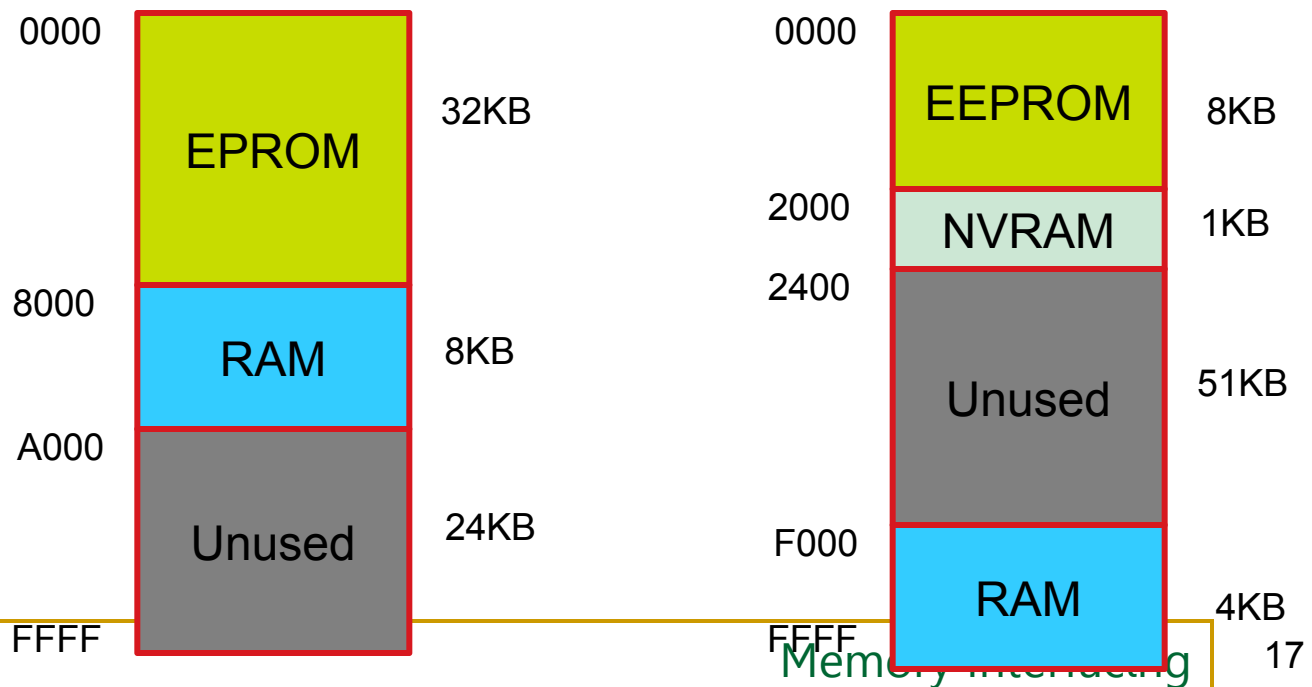- Address space
 - The set of all addresses that can be accessed by a microprocessor
- Address space partitioning
 - A microprocessor is generally interfaced to several memory chips
 - Address space should be partitioned into subsets
 - Each chip should be mapped to a subset (address mapping)
- Examples




Memory Mapping

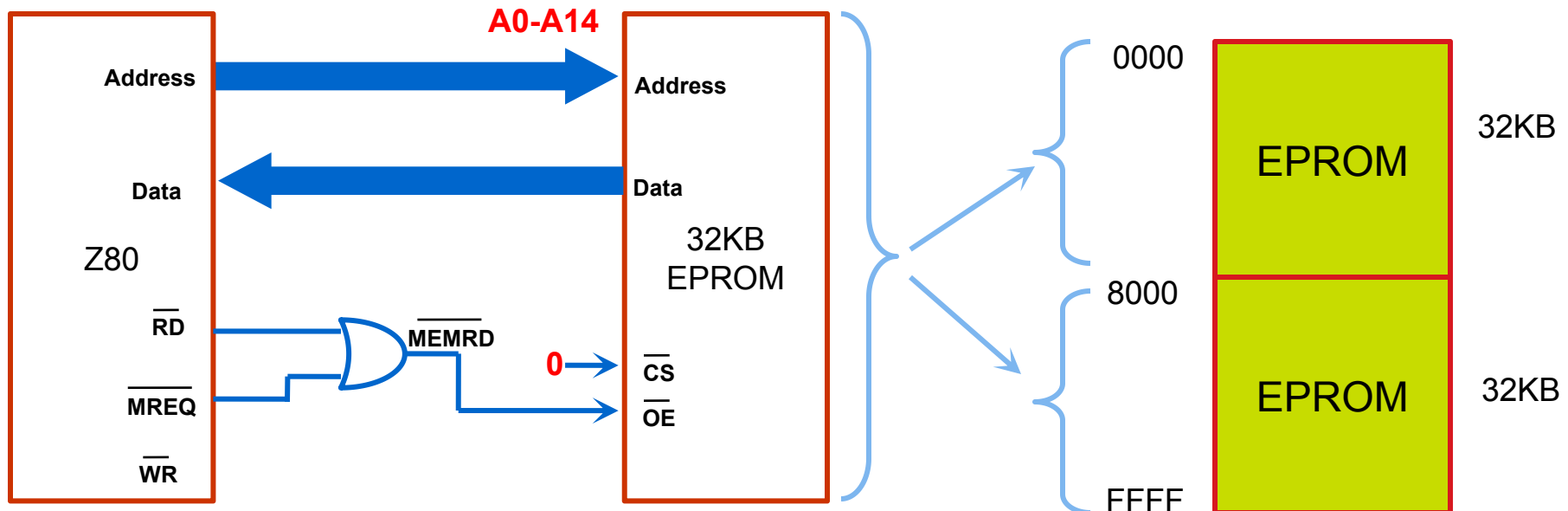
- Let's always keep the chip selected
 - Memory chip is mapped multiple times
 - An address decoder eliminates this behavior
 - Input: high order bits of address
 - Output: Chip-select signals
 - May be ignored if we need simpler designs



Memory Mapping

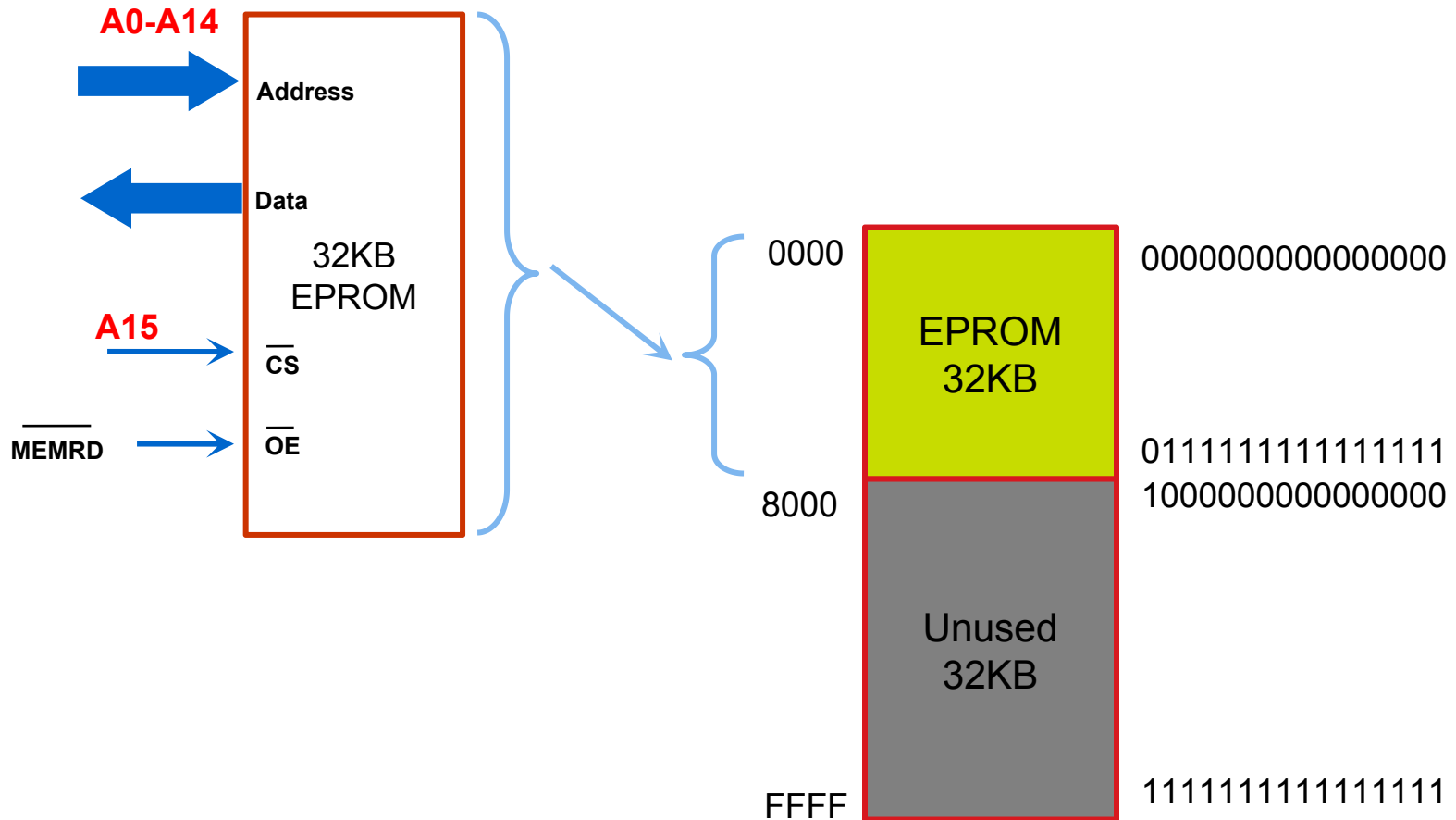


Memory Mapping

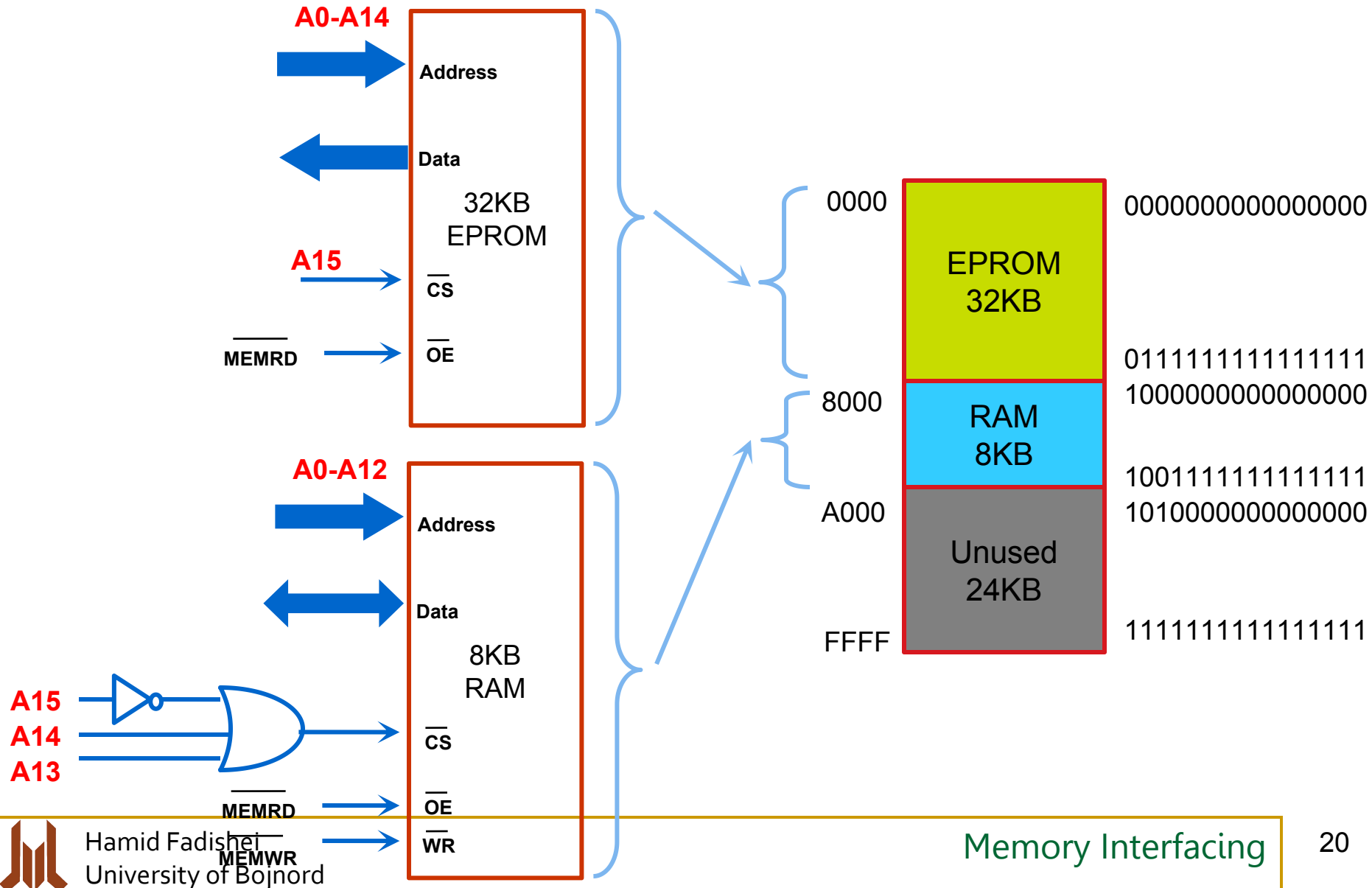

Memory Mapping

- Address decoder

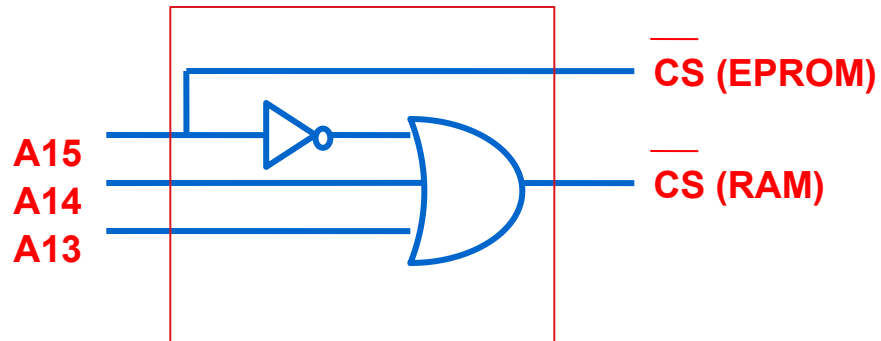

Some part numbers

■ SRAM

- 6116

- 16 Kbits (2KBytes) static RAM

■ EPROM

- 2764

- 64 Kbits (8KBytes) EPROM

■ EEPROM

- AT28C256

- 256 Kbits (64KBytes) EEPROM

■ NVRAM


- M48Z02

- 2KBytes NVRAM




Address decoding chips

- 74138 3-to-8 decoder

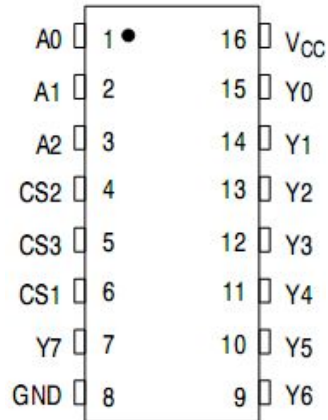


Inputs						Outputs							
CS1	CS2	CS3	A2	A1	A0	Y0	Y1	Y2	Y3	Y4	Y5	Y6	Y7
X	X	H	X	X	X	H	H	H	H	H	H	H	H
X	H	X	X	X	X	H	H	H	H	H	H	H	H
L	X	X	X	X	X	H	H	H	H	H	H	H	H
H	L	L	L	L	L	L	H	H	H	H	H	H	H
H	L	L	L	L	H	H	L	H	H	H	H	H	H
H	L	L	L	H	L	H	H	L	H	H	H	H	H
H	L	L	L	H	H	H	H	L	H	H	H	H	H
H	L	L	H	H	L	H	H	H	H	H	H	L	H
H	L	L	H	H	H	H	H	H	H	H	H	H	L

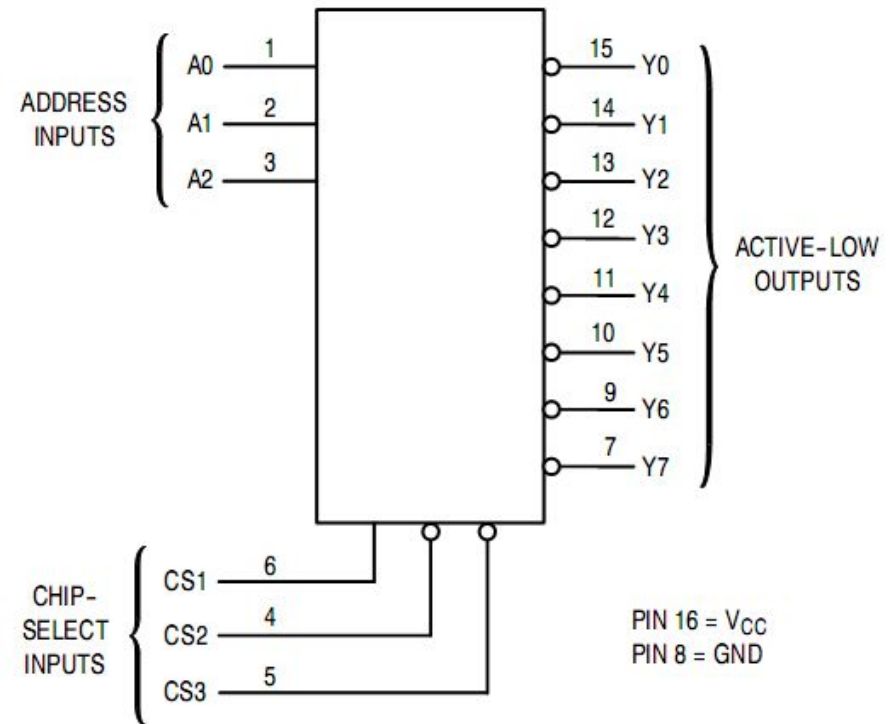


Address decoding chips

- 74139 dual 2-to-4 decoder

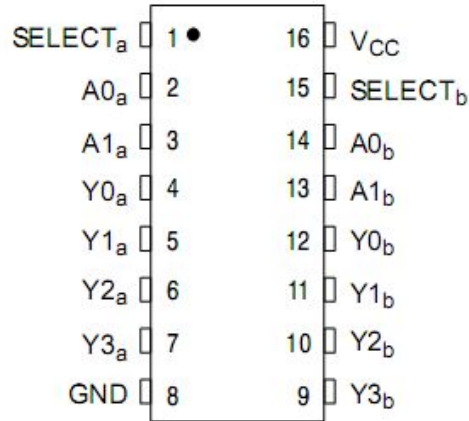

Inputs			Outputs			
Select	A1	A0	Y0	Y1	Y2	Y3
H	X	X	H	H	H	H
L	L	L	L	H	H	H
L	L	H	H	L	H	H
L	H	L	H	H	L	H
L	H	H	H	H	H	L

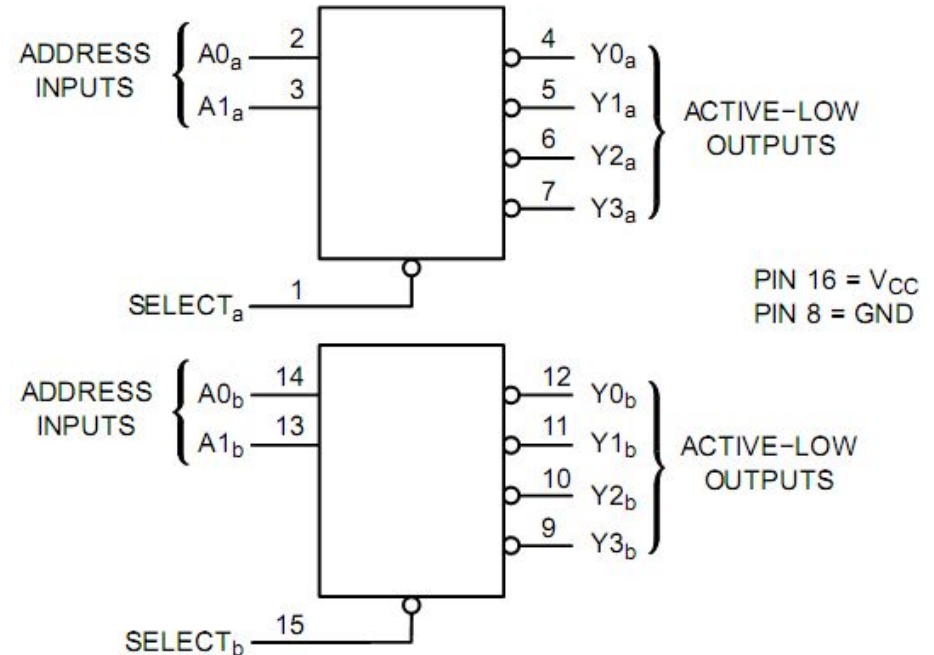


Address decoding chips

- Example usage


- In what range is the 2732 mapped?

- 1000-1FFF

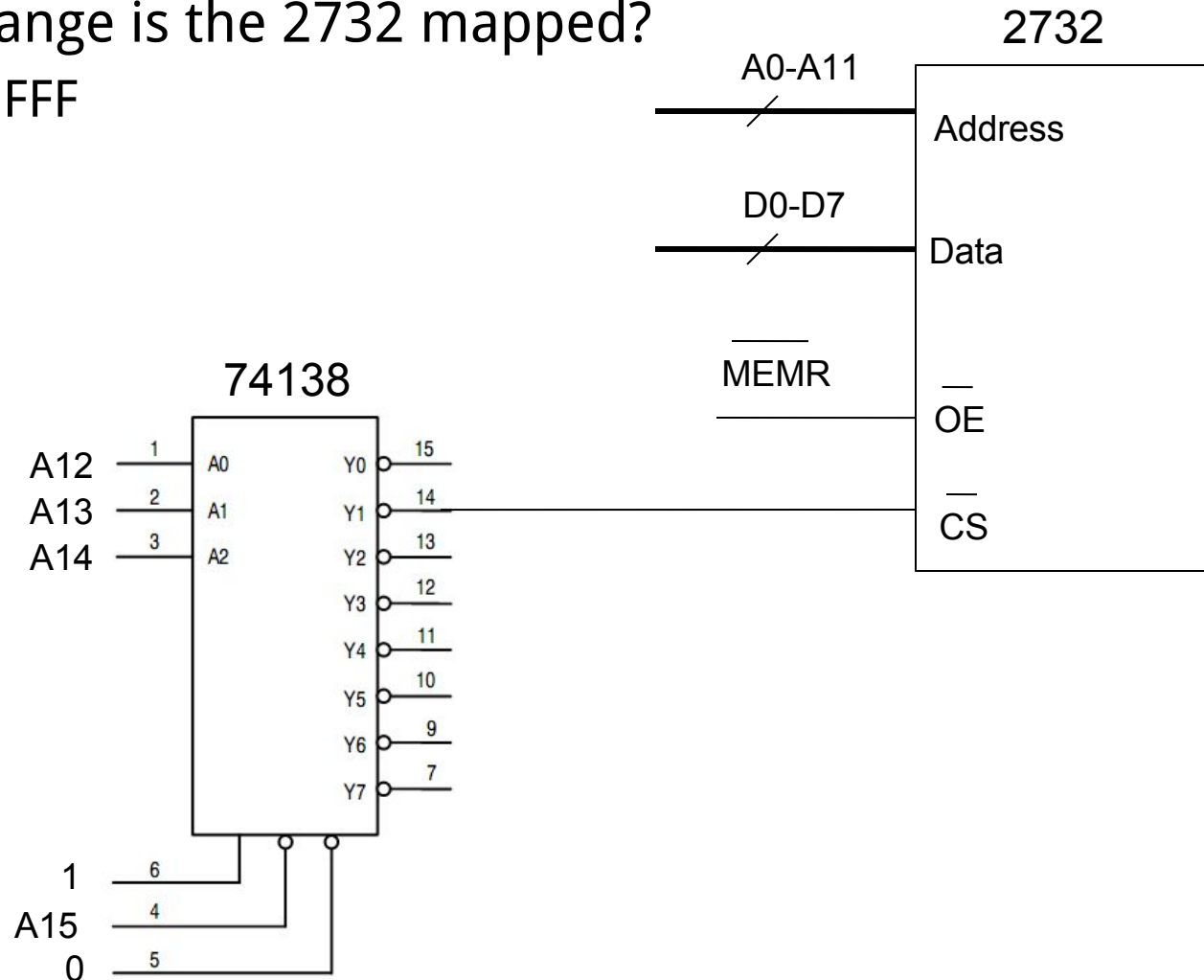


Slow memories

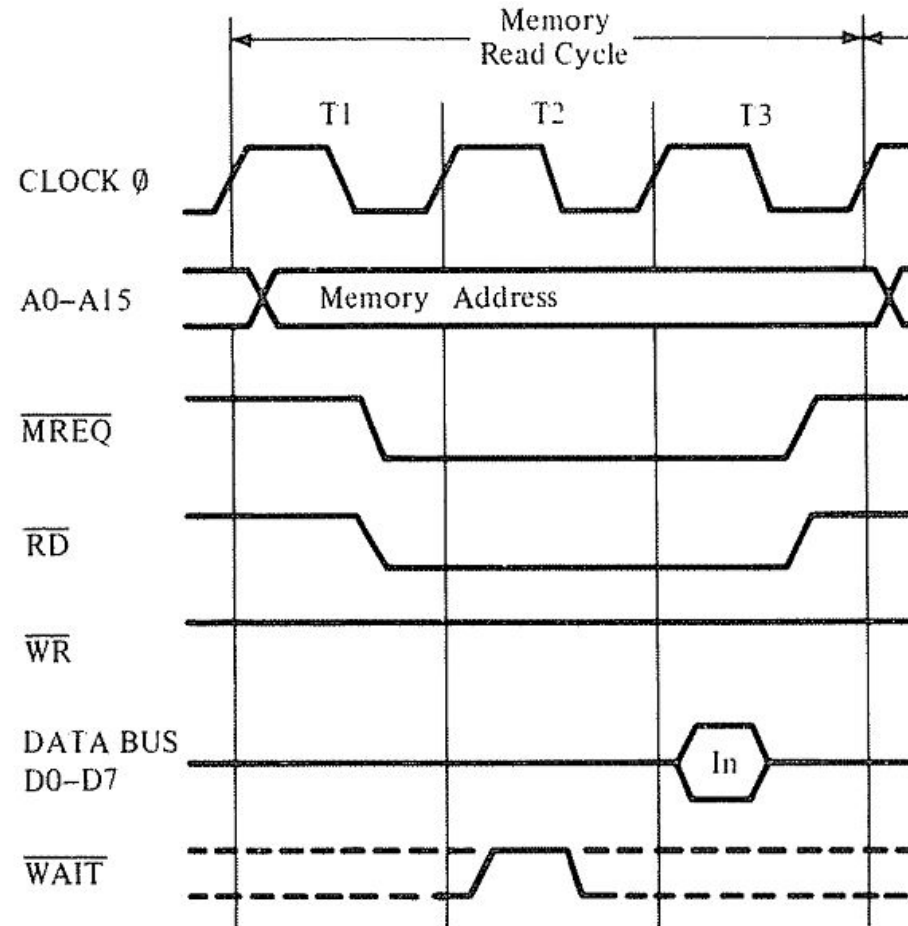- Let's look again at Z80 memory timing
 - ❑ waits less than 2 clock cycles for memory
 - ❑ What if memory access time is longer?
- Adding wait states
 - ❑ You should assert WAIT in T2
 - ❑ Then Z80 will add a wait state T_w
 - ❑ You may keep WAIT active extra wait states



Slow memories

■ Read/Write with wait states

 

Slow memories

- Adding one wait state to each memory cycle

